Practice Question Set For GCSE
Subject : Physics
Paper-1 Topic: Electricity (Low Demand)

Merit Minds
www.merit-minds.com
Exam Preparation and Free Resources

Name of the Student:_____
Max. Marks : 16 Marks **Time : 16 Minutes**

Q1.

Each letter, **A**, **B**, **C**, **D** and **E**, represents an energy transformation.

A electrical to chemical
B electrical to heat
C electrical to kinetic
D electrical to light
E electrical to sound

Match each of the following devices to the useful energy transformation that the device is designed to make.

Write the correct letter, **A**, **B**, **C**, **D** or **E**, in the box below each device.

Use each letter no more than once.

Fan	**Kettle**	**Lamp**	**Radio**
		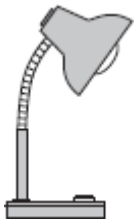	
☐	☐	☐	☐

(Total 4 marks)

Q2.

(a) The diagram shows the energy transformations produced by a television.

Downloaded from www.merit-minds.com

When the television is working, 1200 joules of energy are supplied to the television every second. The useful energy transferred by the television is 720 joules every second.

(i) Use the equation in the box to calculate the efficiency of the television.

$$\text{efficiency} = \frac{\text{useful energy transferred by the device}}{\text{total energy supplied to the device}}$$

Show clearly how you work out your answer.

_____

_____

Efficiency = _____

(2)

(ii) Use **one** word from the diagram to complete the following sentence.

The electrical energy that is **not** usefully transformed by the television is

wasted as _____ .

(1)

(b) A homeowner is sent an electricity bill every 3 months. The total amount of electrical energy used during one 3-month period was 800 kilowatt-hours.
Electrical energy costs 15p per kilowatt-hour.

Use the equation in the box to calculate the cost of the energy transferred from the mains electricity supply.

total cost = number of kilowatt-hours × cost per kilowatt-hour

Show clearly how you work out your answer and give the unit.

_____

_____

Cost = _____

(2)

(Total 5 marks)

Downloaded from www.merit-minds.com

Q3.

(a) The diagram shows the circuit that a student used to investigate how the current through a resistor depends on the potential difference across the resistor.

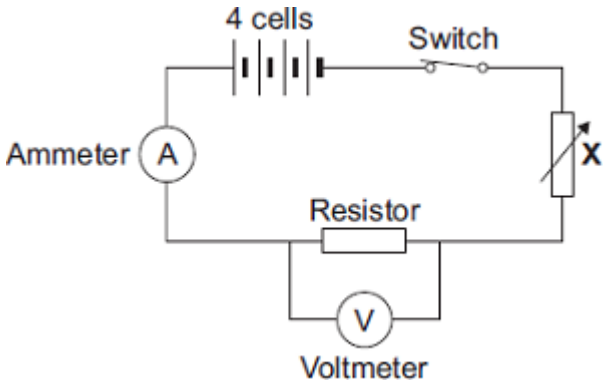

(i) Each cell provides a potential difference of 1.5 volts.

What is the total potential difference provided by the four cells in the circuit?

_____

Total potential difference = _____ volts

(1)

(ii) The student uses the component labelled **X** to change the potential difference across the resistor.

What is component **X**?

Draw a ring around your answer.

light-dependent resistor **thermistor** **variable resistor**

(1)

(iii) Name a component connected in parallel with the resistor.

_____

(1)

(b) The results obtained by the student have been plotted on a graph.

Downloaded from www.merit-minds.com

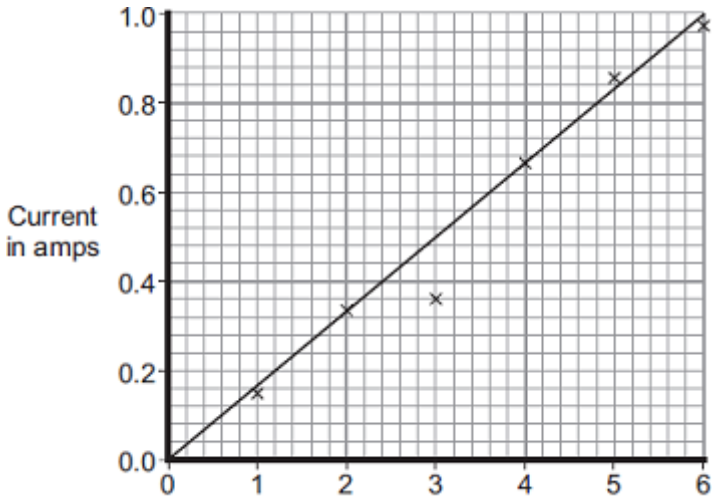

(i) One of the results is anomalous.

Draw a ring around the anomalous result.

(1)

(ii) Which **one** of the following is the most likely cause of the anomalous result?

Put a tick (✓) in the box next to your answer.

The student misread the ammeter. ☐

The resistance of the resistor changed. ☐

The voltmeter had a zero error. ☐

(1)

(iii) What was the interval between the potential difference values obtained by the student?

_____

_____

(1)

(c) Describe the relationship between the potential difference across the resistor and the current through the resistor.

_____

_____

(1)

(Total 7 marks)

Downloaded from www.merit-minds.com